

The World Leader in High-Performance Signal Processing Solutions



Switching Amplifiers; The Gap between Theory and Practical Circuits

Bob Adams
Analog Devices Inc
Dec 4, 2003



History

- ◆ Switching amplifiers have been around for many years.
- ◆ Quality and reliability of early units was very bad. They were used mostly for space-efficient high-power amplifiers.
- ◆ Recently, flat-panel TV's and multi-channel surround amplifiers have started a new wave of interest in Switching amplifiers.
- ◆ Many designers are now “re-discovering” all the challenges of switching amplifiers.


What has Changed?

- ◆ **Market requirement for space-efficient amplifiers**
 - 6-channel surround amplifiers
 - Flat-panel displays
- ◆ **DMOS, VMOS power transistors**
 - Reliable (no secondary breakdown)
 - Cheap
 - DMOS can be integrated with conventional CMOS processes
- ◆ **New modulation algorithms**
 - More complex switching algorithms avoid large spectral sticks at carrier frequency (good for EMI)
 - Feedback architectures reduce distortion and noise with real-world power supplies.

Design Approaches

- ◆ **PWM**
- ◆ **Sigma-Delta**
- ◆ **Analog Modulators**
- ◆ **Digital Modulators**
- ◆ **Open-loop versus Closed-loop**
- ◆ **Power-Stage-Only Feedback**

PWM

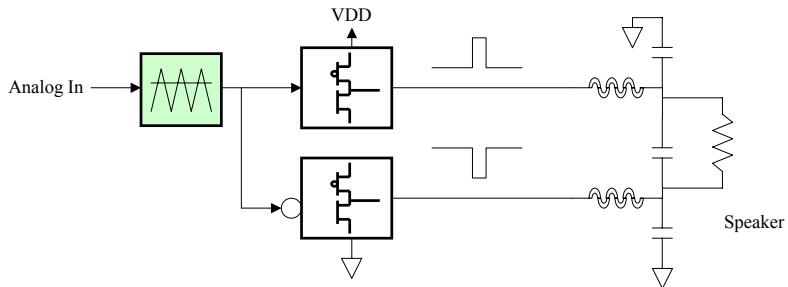

◆ Drawbacks

- If switching rate is too low, non-harmonic distortion is produced by carrier sidebands
- Bad EMI due to strong component at the switching frequency


5

Switching Amplifier, December - 4 - 2003



PWM

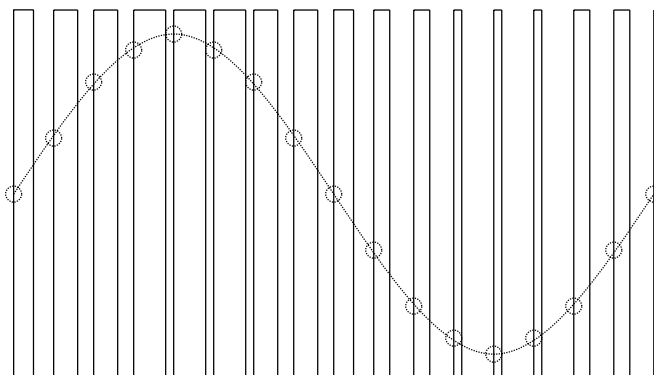The pulse sequence is the PWM representation of the output signal.




6

Switching Amplifier, December - 4 - 2003



PWM EMI Performance

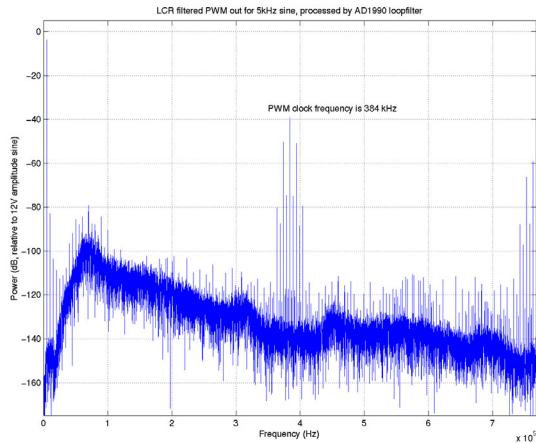

7

Switching Amplifier, December - 4 - 2003



Design Approaches


- ◆ PWM
- ◆ **Sigma-Delta**
- ◆ Analog Modulators
- ◆ Digital Modulators
- ◆ Open-loop versus Closed-loop
- ◆ Power-Stage-Only Feedback

8

Switching Amplifier, December - 4 - 2003



Sigma-Delta

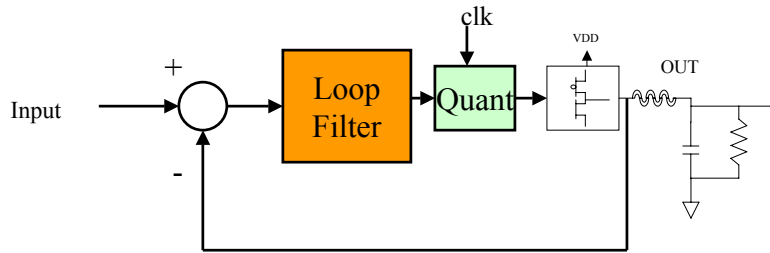

◆ Advantages

- Very low distortion from modulation technique
- Output stage is inside the feedback loop
- Low EMI due to random behavior of switching

◆ Disadvantages


- High transition rate reduces efficiency (must be specially designed to reduce transition rate)
- Random nature of switching causes bad SNR unless the output stage is inside the feedback loop.

9

Switching Amplifier, December - 4 - 2003



Sigma-Delta in the Time Domain

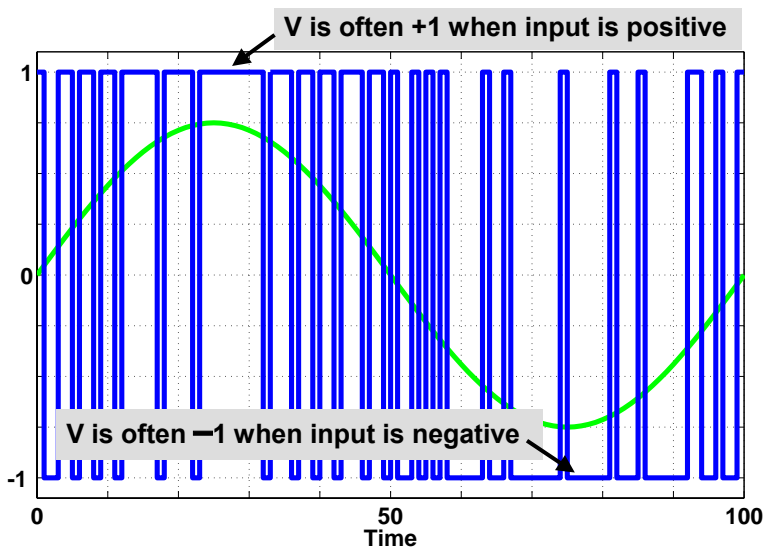


10

Switching Amplifier, December - 4 - 2003



Sigma-Delta in the Frequency Domain

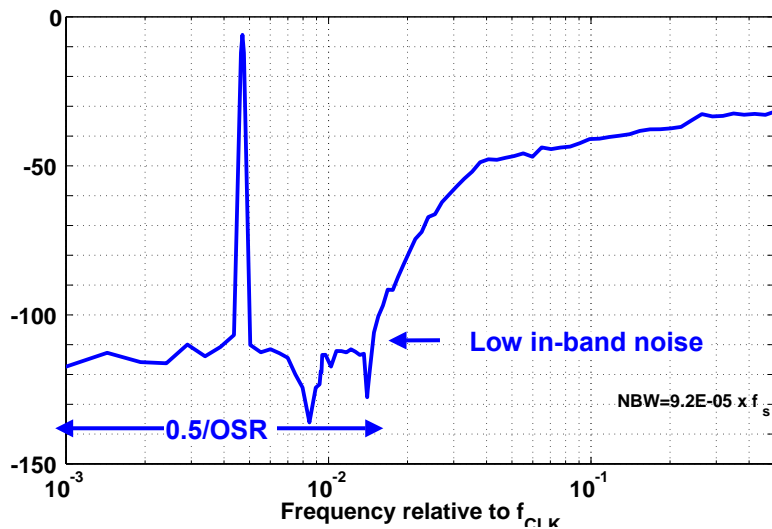

11

Switching Amplifier, December - 4 - 2003



Design Approaches

- ◆ PWM
- ◆ Sigma-Delta
- ◆ **Analog Modulators**
- ◆ Digital Modulators
- ◆ Open-loop versus Closed-loop
- ◆ Power-Stage-Only Feedback

12

Switching Amplifier, December - 4 - 2003



Analog Modulator


◆ Advantages

- Allows an inexpensive closed-loop system to be built, giving improved performance.
- Switching can occur anywhere (not limited to a clock edge).

◆ Disadvantages

- Needs a D/A converter if input signal is digital
- Difficult to integrate on very small processes like 0.13u.

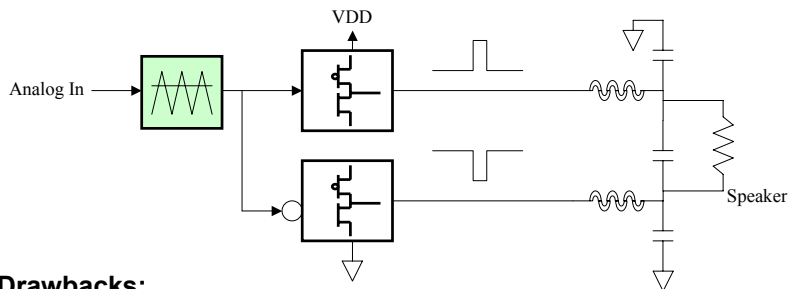Analog PWM Modulator with Open-loop Output Stage



◆ Drawbacks:

- Output stage is open-loop
- Output stage behavior during “non-overlap” time causes noise and distortion
- Supply must be regulated (0 dB supply rejection!)
- Has theoretic distortion from the PWM process

Design Approaches


- ◆ PWM
- ◆ Sigma-Delta
- ◆ Analog Modulators
- ◆ **Digital Modulators**
- ◆ Open-loop versus Closed-loop
- ◆ Power-Stage-Only Feedback

15

Switching Amplifier, December - 4 - 2003



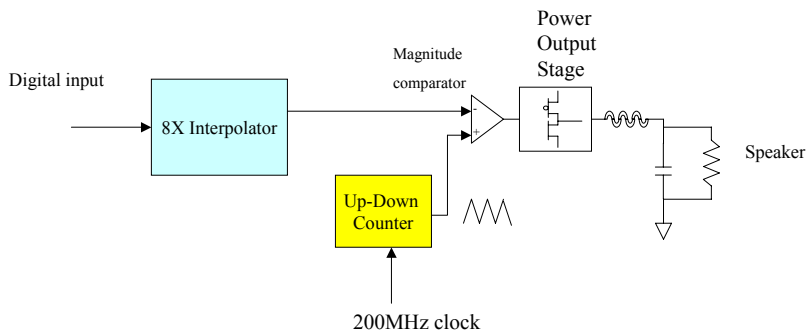Digital PWM amps with open-loop Output Stage




- ◆ **Problem:**
 - The number of possible pulse widths is quantized to about 600 widths.
 - The oversampling factor is only 8X, so with a 200MHz clock you only have an 11-bit system.

16

Switching Amplifier, December - 4 - 2003



Digital PWM amp with Noise-Shaping Loops

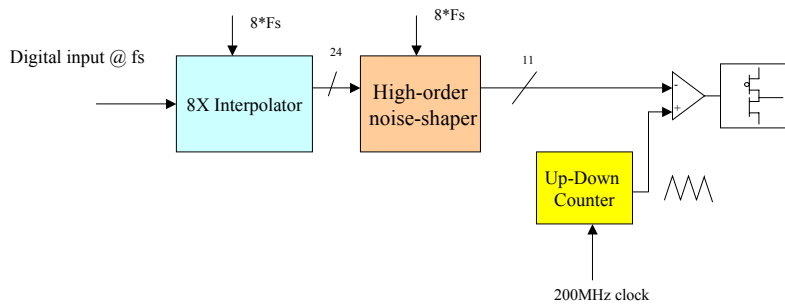

- ◆ Using a noise-shaper improves the SNR.
- ◆ The oversampling factor is only 8, so the improvement at 20KHz is not very good.

17

Switching Amplifier, December - 4 - 2003



Design Approaches

- ◆ PWM
- ◆ Sigma-Delta
- ◆ Analog Modulators
- ◆ Digital Modulators
- ◆ Open-loop versus Closed-loop
- ◆ Power-Stage-Only Feedback

18


Switching Amplifier, December - 4 - 2003




Open-loop Designs

“Real-world” Experience


1) *Initial Design*

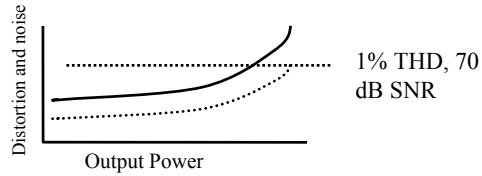

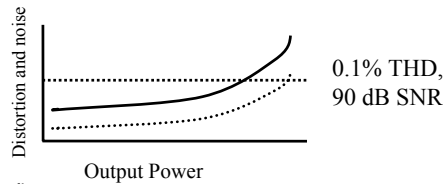2) *After 2 years of re-design, under ideal laboratory conditions*



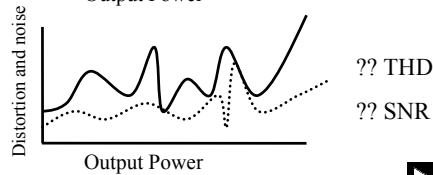3) *In real customer system, with real power supply and over large temperature and process variations*




19

Switching Amplifier, December - 4 - 2003



Closed-loop designs (Analog)

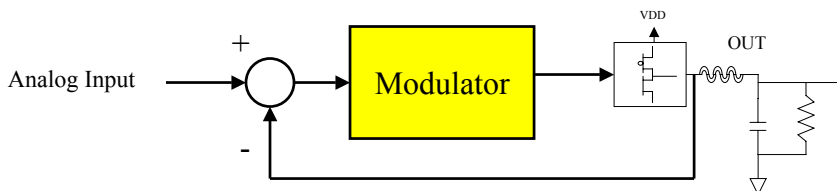

◆ Advantages

- PSRR, distortion and noise are all improved by the feedback gain.
- Less sensitive to process shifts, changes in non-overlap time, etc.

◆ Challenges

- Difficult to stabilize high-order designs
- Must use special design techniques to make sure close to 100% modulation can be reached (otherwise MAX power is reduced)

20

Switching Amplifier, December - 4 - 2003




Design Approaches

- ◆ PWM
- ◆ Sigma-Delta
- ◆ Analog Modulators
- ◆ Digital Modulators
- ◆ Open-loop versus Closed-loop
- ◆ **Power-Stage-Only Feedback**

Power-Stage-Only Feedback

- ◆ A separate modulator, either analog or digital;
- ◆ Feedback around the **POWER STAGE** to shape the errors from the power stage. The shaping is done by **ADJUSTING THE EDGE LOCATIONS** from the modulator.

Power-stage feedback only (Digital Mod)

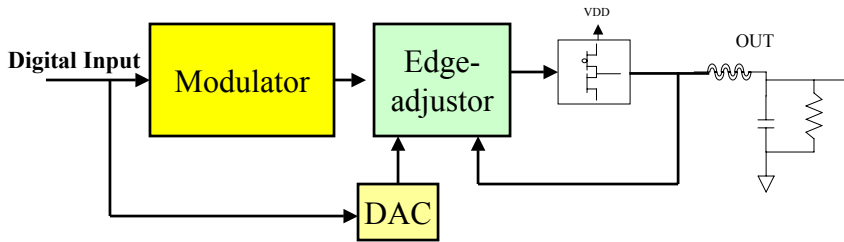

◆ Advantages

- High-order modulator can be all-digital
- Power-stage errors are shaped independently using a separate loop that adjusts only the edge positions of the main modulator.

Conclusions

- ◆ There are a very large number of different topologies to consider
- ◆ Real-world problems include efficiency, EMI, PSRR, and other output-stage non-linearities.
- ◆ Open-loop PWM systems are not well-suited to solve real-world problems.
- ◆ Best topologies use some form of analog feedback.

Additional Material

Why Switching Amplifiers did not succeed 30 years ago

- ◆ **Market Reasons**
 - Most amplifiers were only 2 channels at modest power. Switching amplifiers had only a small size/weight advantage, except at very high power.
- ◆ **Technical reasons**
 - Poor reliability. Bipolar power transistors have secondary breakdown problems.
 - Poor performance. THD+N and SNR limited by open-loop switching stage design.
 - Bad EMI. Simple PWM modulators make strong tones at the switching frequency.


Digital Modulators

- ◆ **Digital modulator is often preferred in modern systems.**
- ◆ **Advantages:**
 - Direct digital input
 - Some DSP compensation of distortion may be possible
- ◆ **Challenges**
 - Hard to close the loop around the power stage (need a fast A/D)
 - Switching must occur on a clock edge (limits modulator performance).

Digital Modulators


- ◆ **Design Choices:**
 - **Digital PWM using High-frequency Clock**
 - ◆ Resolution limited by clock speed (finite number of pulse widths)
 - **Digital PWM with digital noise-shaping loop**
 - ◆ Oversampling factor is not very high (8x)
 - **Digital Sigma-Delta Modulator**
 - ◆ Transition rate is too high, need some way of reducing it.

Theoretic PWM Distortion

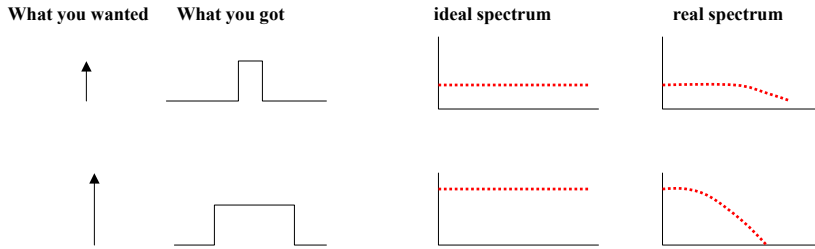


- ◆ High frequency signal components are modulated by the sinc(x) response of the variable-width pulse.
- ◆ Various compensation schemes have been proposed.

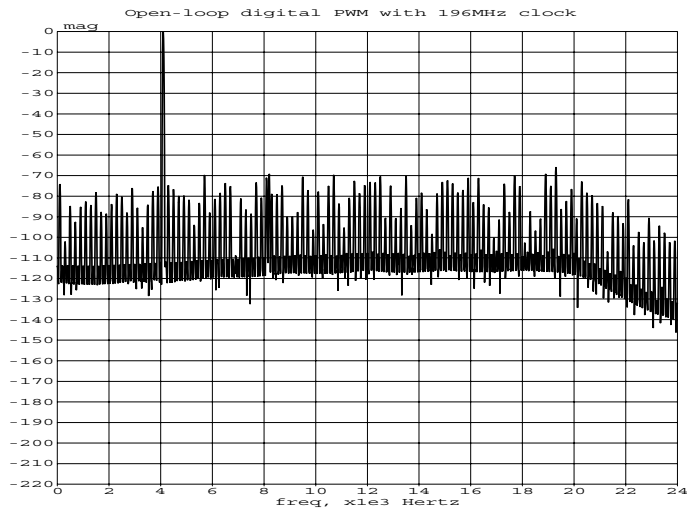Sim for digital amp with 196MHz clock, no feedback



Example STF and NTF

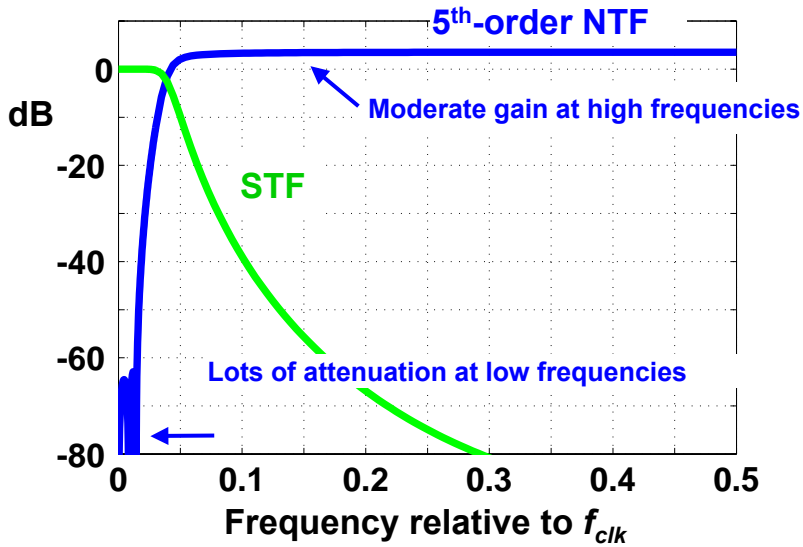


31

Switching Amplifier, December - 4 - 2003



Closed-loop Design (Digital)

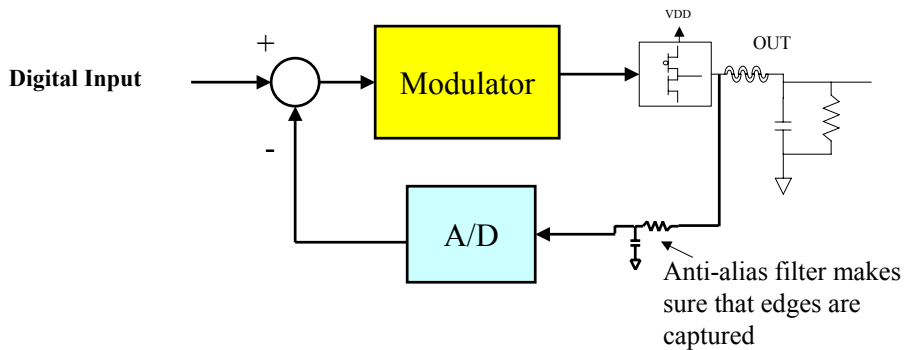

◆ Challenges

- A/D must have full resolution of desired SNR
- A/D must have very low latency
- A/D must have a filter to anti-alias the edge behavior.

32

Switching Amplifier, December - 4 - 2003

